

Федеральное государственное бюджетное образовательное учреждение  
высшего профессионального образования

**Национальный исследовательский университет «МЭИ»**  
**Институт информационных и вычислительных технологий**

---

**Кафедра Вычислительных технологий**

**Арифметико-логическое устройство.**

**Моделирование**

**курсовой работы по курсу «Функциональные узлы и процессоры»**

**Выполнил:**

Студент: Архипов Д. Г.

Группа: А-06-21

Вариант 1

**Проверил:**

Ключников А. М.

**Москва 2024**

## 1. Задание на курсовую работу

Цель: разработать схему арифметико-логического устройства (АЛУ), осуществляющую:

- 1) алгебраическое сложение двух многоразрядных чисел А и В в заданном коде (МДК или МОК);
- 2) операцию \* над суммой чисел А и В.

Числа А и В поступают в АЛУ в нормализованном виде параллельным модифицированным прямым кодом на входы многоразрядных регистров RGA и RGB.

Результат алгебраического сложения передается в регистр RGS.

Перед выполнением операции алгебраического сложения числа А и В, заданные в модифицированном прямом коде, должны быть предварительно преобразованы в заданный код.

В сумматоре МДК входной перенос поступает извне, а выходной перенос не используется.

### Исходные данные:

- Серия элементов: 155
- Вид операции \*:  
Выделение признака: необходима нормализация вправо
- Тип сумматора: МДК
- Разрядность SM: 12
- $T_{\text{max зад SM}}$ : 148 нс

Провести расчеты:

- 1) Задержку самого длинного тракта SM;
- 2) Расчет тактовой частоты.

## 2. Разработка структурной схемы АЛУ

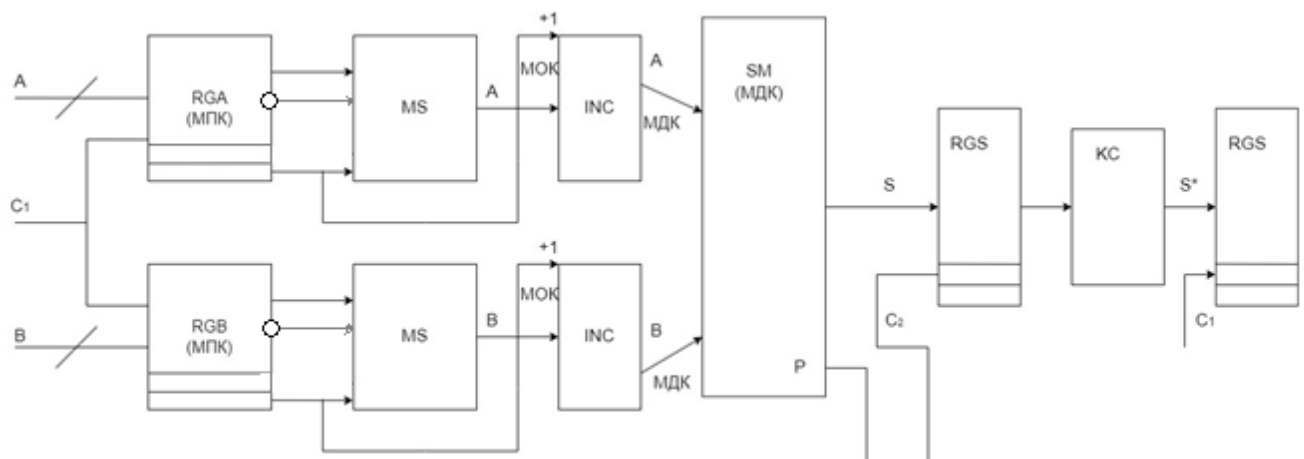


Рисунок 1. Структурная схема АЛУ

Обозначения на схеме:

A, B – многоразрядные числа,

RGA – регистр числа A,

RGB – регистр числа B,

MS – мультиплексор,

SM – сумматор,

INC – инкрементор,

RGS – регистр результата сложения A и B и поиска старшего разряда,

KC – комбинационная схема,

RGS\* – регистр конечного результата,

C<sub>1</sub> и C<sub>2</sub> – синхросигналы,

S, S\* - значения суммы,

МПК – модифицированный прямой код,

МДК – модифицированный дополнительный код.

Принцип работы: на входы регистров RGA и RGB подаются двенадцатиразрядные сигналы A и B в прямом модифицированном коде. С управляющего устройства подаются синхросигналы C<sub>1</sub> и C<sub>2</sub>. Мультиплексор

MS и инкрементор INC преобразуют модифицированный прямой код в модифицированный дополнительный код. Далее числа складываются в сумматоре SM, где проводится операция выделения признака: нормализация вправо. Результат операции записывается в RGS.

### 3. Разработка регистра

Для создания регистра будут использованы D-триггеры типа «защелка». Для реализации 12-разрядных чисел понадобится 3 набора триггеров K155TM7.

Функциональная схема регистра представлена на рисунке 2.

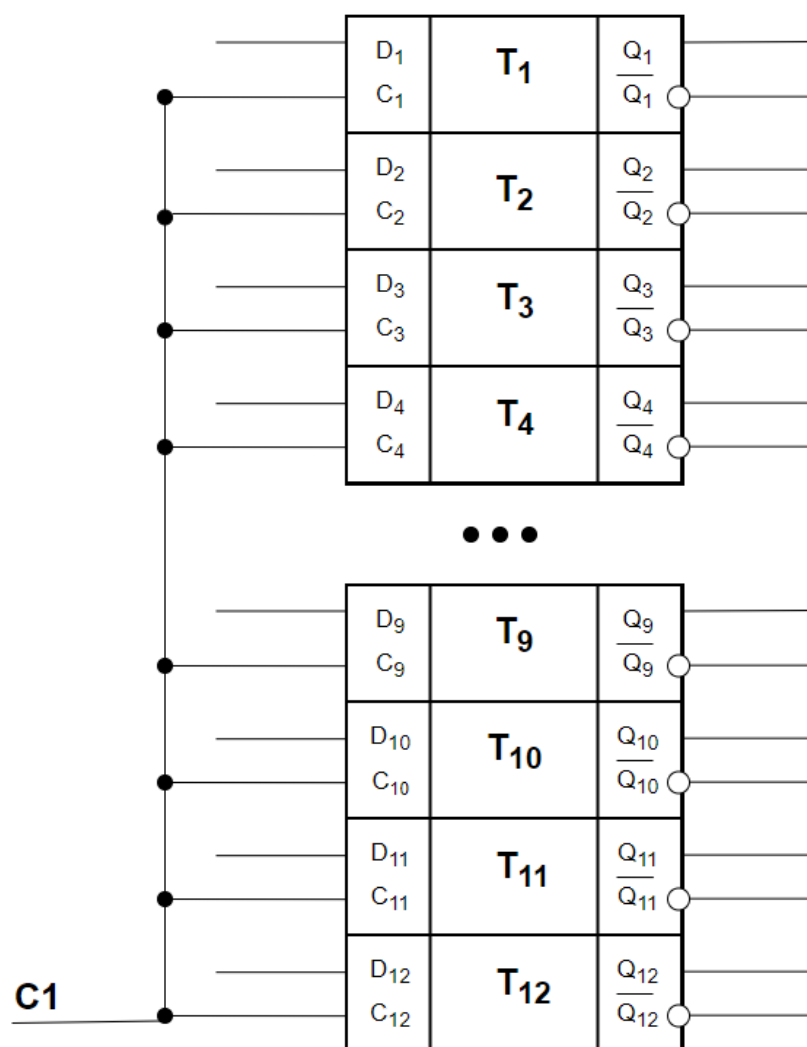


Рисунок 2. Функциональная схема регистра

Задержка регистра:  $T_{reg} = 40$  нс

Реализация регистра и микросхемы K155TM7 на VHDL представлена ниже.

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity K155TM7 is
  port(C: in std_logic; D: in std_logic_vector(3 downto 0); Q: out std_logic_vector(3 downto 0));
end K155TM7;

Architecture arch_K155TM7 of K155TM7 is
  begin process(C, D(3 downto 0))
    begin
      if (C='1') then
        Q(3 downto 0) <= D(3 downto 0) after 40 ns;
      end if;
    end process;
  end arch_K155TM7;

#-----#

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity K155TM7_scheme_12digits is
  port(C: in std_logic; D: in std_logic_vector(11 downto 0); Q: out std_logic_vector(11 downto 0));
end K155TM7_scheme_12digits;

Architecture arch_K155TM7_scheme_12digits of K155TM7_scheme_12digits is
  component K155TM7 is
    port(C: in std_logic; D: in std_logic_vector(3 downto 0); Q: out std_logic_vector(3 downto 0));
  end component K155TM7;

  begin
    RG1: K155TM7 port map (C, D(3 downto 0), Q(3 downto 0));
    RG2: K155TM7 port map (C, D(7 downto 4), Q(7 downto 4));
    RG3: K155TM7 port map (C, D(11 downto 8), Q(11 downto 8));

  end arch_K155TM7_scheme_12digits;
```

#### 4. Синтез элементов россыпи

Ниже представлена реализация элементов 1И-НЕ, 2И-НЕ, 3И-НЕ, 4И-НЕ, 5И-НЕ, 6И-НЕ, 7И-НЕ, 2И-2ИЛИ-НЕ, а также вспомогательных функций PI (прозрачности) и GEN (генерации).

Задержки всех элементов типа И-НЕ, И-ИЛИ-НЕ составляют 17.5 нс.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

```

```

Entity NAND1 is
    Generic (T: time:=17.5 ns);
    Port(x1: in std_logic; y: out std_logic);
End NAND1;

```

```

Architecture arch_NAND1 of NAND1 is
Begin
    y<=NOT x1 after T;
end arch_NAND1;

```

#-----#

```

Entity NAND2 is
    Generic (T: time:=17.5 ns);
    Port(x1,x2: in std_logic; y: out std_logic);
End NAND2;

```

```

Architecture arch_NAND2 of NAND2 is
Begin
    y<=NOT(x1 AND x2) after T;
end arch_NAND2;

```

#-----#

```

Entity NAND3 is
    Generic (T: time:=17.5 ns);
    Port(x1,x2,x3: in std_logic; y: out std_logic);
End NAND3;

```

```

Architecture arch_NAND3 of NAND3 is
Begin
    y<=NOT(x1 AND x2 AND x3) after T;
end arch_NAND3;

```

#-----#

```

Entity NAND4 is
    Generic (T: time:=17.5 ns);
    Port(x1,x2,x3,x4: in std_logic; y: out std_logic);
End NAND4;

```

```

Architecture arch_NAND4 of NAND4 is
Begin
    y<=NOT(x1 AND x2 AND x3 AND x4) after T;
end arch_NAND4;

```

#-----#

```

Entity NAND5 is
    Generic (T: time:=17.5 ns);
    Port(x1,x2,x3,x4,x5: in std_logic; y: out std_logic);
End NAND5;

```

Architecture arch\_NAND5 of NAND5 is

Begin

    y<=NOT(x1 AND x2 AND x3 AND x4 AND x5) after T;  
end arch\_NAND5;

#-----#

Entity NAND6 is

    Generic (T: time:=17.5 ns);

    Port(x1,x2,x3,x4,x5,x6: in std\_logic; y: out std\_logic);

End NAND6;

Architecture arch\_NAND6 of NAND6 is

Begin

    y<=NOT(x1 AND x2 AND x3 AND x4 AND x5 AND x6) after T;  
end arch\_NAND6;

#-----#

Entity NAND7 is

    Generic (T: time:=17.5 ns);

    Port(x1,x2,x3,x4,x5,x6,x7: in std\_logic; y: out std\_logic);

End NAND7;

Architecture arch\_NAND7 of NAND7 is

Begin

    y<=NOT(x1 AND x2 AND x3 AND x4 AND x5 AND x6 AND x7) after T;  
end arch\_NAND7;

#-----#

library ieee;

use ieee.std\_logic\_1164.all;

use ieee.std\_logic\_arith.all;

use ieee.std\_logic\_unsigned.all;

Entity PI is

    Generic (T: time:=35 ns);

    Port(x1,x2: in std\_logic; y: out std\_logic);

End PI;

Architecture arch\_PI of PI is

Begin

    y<= (x1 OR x2) after T;  
end arch\_PI;

#-----#

Entity GEN is

    Generic (T: time:=35 ns);

    Port(x1,x2: in std\_logic; y: out std\_logic);

End GEN;

Architecture arch\_GEN of GEN is

```

Begin
    y<= (x1 AND x2) after T;
end arch_GEN;

```

## 5. Сумматор

### 5.1 II ярус сумматора

Разобьем разряды на 2 группы: 2 группы по 6 разрядов.

Используются 2 функции:

$$1) \quad \Gamma_i = a_i \cdot b_i \qquad 2) \quad \pi_j = a_i \vee b_i$$

 


Рисунок 3. Схемы блоков генерации и прозрачности

На VHDL для удобства  $\Gamma$  и  $\Pi$  рассчитываются заранее и используются на 1х и 2х ярусах.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity PI_and_GEN is
    port(A, B: in std_logic_vector(11 downto 0); PI_out, GEN_out: out std_logic_vector(11 downto 0));
end PI_and_GEN;

architecture arch_PI_and_GEN of PI_and_GEN is

    component PI is
        port(x1,x2: in std_logic; y: out std_logic);
    end component PI;

    component GEN is
        port(x1,x2: in std_logic; y: out std_logic);
    end component GEN;

begin

    PI1: PI port map(A(0), B(0), PI_out(0));
    PI2: PI port map(A(1), B(1), PI_out(1));
    PI3: PI port map(A(2), B(2), PI_out(2));
    PI4: PI port map(A(3), B(3), PI_out(3));
    PI5: PI port map(A(4), B(4), PI_out(4));

```



```

PI6: PI port map(A(5), B(5), PI_out(5));
PI7: PI port map(A(6), B(6), PI_out(6));
PI8: PI port map(A(7), B(7), PI_out(7));
PI9: PI port map(A(8), B(8), PI_out(8));
PI10: PI port map(A(9), B(9), PI_out(9));
PI11: PI port map(A(10), B(10), PI_out(10));
PI12: PI port map(A(11), B(11), PI_out(11));

GEN1: GEN port map(A(0), B(0), GEN_out(0));
GEN2: GEN port map(A(1), B(1), GEN_out(1));
GEN3: GEN port map(A(2), B(2), GEN_out(2));
GEN4: GEN port map(A(3), B(3), GEN_out(3));
GEN5: GEN port map(A(4), B(4), GEN_out(4));
GEN6: GEN port map(A(5), B(5), GEN_out(5));
GEN7: GEN port map(A(6), B(6), GEN_out(6));
GEN8: GEN port map(A(7), B(7), GEN_out(7));
GEN9: GEN port map(A(8), B(8), GEN_out(8));
GEN10: GEN port map(A(9), B(9), GEN_out(9));
GEN11: GEN port map(A(10), B(10), GEN_out(10));
GEN12: GEN port map(A(11), B(11), GEN_out(11));

end arch_PI_and_GEN;

```

 


Рисунок 4. II ярус двухъярусного сумматора

Выходной перенос из  $j$ -ой группы равен:

$$E_j = e_{j+1} = \Gamma_j \vee e_j \Pi_j$$

Система уравнений:

$$\begin{cases} e_1 = g \\ E_1 = e_2 = \Gamma_1 \vee e_1 \Pi_1 = \Gamma_6 \vee \Gamma_5 \pi_6 \vee \Gamma_4 \pi_6 \pi_5 \vee \dots \vee \Gamma_1 \pi_6 \pi_5 \pi_4 \pi_3 \pi_2 \vee g \pi_6 \dots \pi_1 \end{cases}$$

где  $\Gamma_i = a_i b_i, \pi_i = a_i \vee b_i$

С помощью формул де Моргана преобразуем систему уравнений:

$$\begin{cases} e_1 = g \\ E_1 = e_2 = \overline{\overline{\Gamma_1} * \overline{e_1 \Pi_1}} = \overline{\overline{\Gamma_6} \cdot \overline{\Gamma_5 \pi_6} \cdot \overline{\Gamma_4 \pi_6 \pi_5} \cdot \dots \cdot \overline{\Gamma_1 \pi_6 \pi_5 \pi_4 \pi_3 \pi_2} \cdot \overline{g \pi_6 \dots \pi_1}} \end{cases}$$

Снизу представлена схема блока переноса 1 группы.

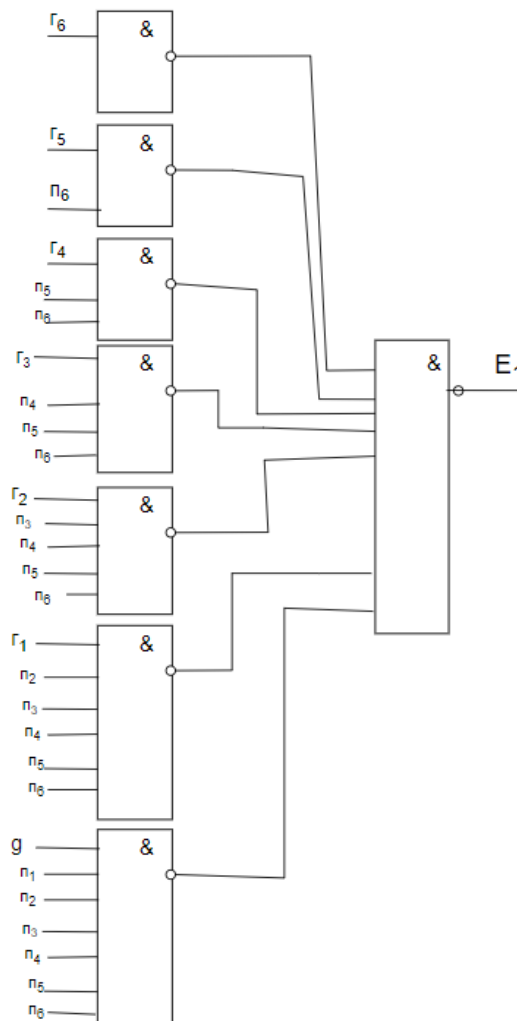


Рисунок 5. Схема блока переноса

Задержка построенного блока переноса II-го яруса равна  $T_{II} = 4 \cdot \tau$

Код для моделирования II-го яруса на VHDL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
```

```

entity Block_carry_II is
  port(g: in std_logic; PI, GEN: in std_logic_vector(5 downto 0); E: out std_logic);
end Block_carry_II;

architecture arch_Block_carry_II of Block_carry_II is
  component NAND1 is
    port(x1: in std_logic; y: out std_logic);
  end component NAND1;

  component NAND2 is
    port(x1, x2: in std_logic; y: out std_logic);
  end component NAND2;

  component NAND3 is
    port(x1, x2, x3: in std_logic; y: out std_logic);
  end component NAND3;

  component NAND4 is
    port(x1, x2, x3, x4: in std_logic; y: out std_logic);
  end component NAND4;

  component NAND5 is
    port(x1, x2, x3, x4, x5: in std_logic; y: out std_logic);
  end component NAND5;

  component NAND6 is
    port(x1, x2, x3, x4, x5, x6: in std_logic; y: out std_logic);
  end component NAND6;

  component NAND7 is
    port(x1, x2, x3, x4, x5, x6, x7: in std_logic; y: out std_logic);
  end component NAND7;

  signal tmp1, tmp2, tmp3, tmp4, tmp5, tmp6, tmp7: std_logic;

begin
  COMP1: NAND1 port map (GEN(5), tmp1);
  COMP2: NAND2 port map (GEN(4), PI(5), tmp2);
  COMP3: NAND3 port map (GEN(3), PI(4), PI(5), tmp3);
  COMP4: NAND4 port map (GEN(2), PI(3), PI(4), PI(5), tmp4);
  COMP5: NAND5 port map (GEN(1), PI(2), PI(3), PI(4), PI(5), tmp5);
  COMP6: NAND6 port map (GEN(0), PI(1), PI(2), PI(3), PI(4), PI(5), tmp6);
  COMP7: NAND7 port map (g, PI(0), PI(1), PI(2), PI(3), PI(4), PI(5), tmp7);
  COMP8: NAND7 port map (tmp1, tmp2, tmp3, tmp4, tmp5, tmp6, tmp7, E);

end arch_Block_carry_II;

```

## 5.2 I ярус сумматора

Составим логические уравнения для реализации параллельного переноса на I ярусе.

$$\left\{ \begin{array}{l} r_1 = e \\ r_2 = r_1 \vee e\pi_1 \\ r_3 = r_2 \vee r_1\pi_2 \vee e\pi_1\pi_2 \\ r_4 = r_3 \vee r_2\pi_3 \vee r_1\pi_2\pi_3 \vee e\pi_1\pi_2\pi_3 \\ r_5 = r_4 \vee r_3\pi_4 \vee r_2\pi_3\pi_4 \vee r_1\pi_2\pi_3\pi_4 \vee e\pi_1\pi_2\pi_3\pi_4 \\ r_6 = r_5 \vee r_4\pi_5 \vee r_3\pi_4\pi_5 \vee r_2\pi_3\pi_4\pi_5 \vee r_1\pi_2\pi_3\pi_4\pi_5 \vee e\pi_1\pi_2\pi_3\pi_4\pi_5 \end{array} \right.$$

Преобразуем эти логические уравнения по закону де Моргана. В

$$\left\{ \begin{array}{l} r_1 = e \\ r_2 = \overline{\overline{r_1} \cdot \overline{e\pi_1}} \\ r_3 = \overline{\overline{r_2} \cdot \overline{r_1\pi_2} \cdot \overline{e\pi_1\pi_2}} \\ r_4 = \overline{\overline{r_3} \cdot \overline{r_2\pi_3} \cdot \overline{r_1\pi_2\pi_3} \cdot \overline{e\pi_1\pi_2\pi_3}} \\ r_5 = \overline{\overline{r_4} \cdot \overline{r_3\pi_4} \cdot \overline{r_2\pi_3\pi_4} \cdot \overline{r_1\pi_2\pi_3\pi_4} \cdot \overline{e\pi_1\pi_2\pi_3\pi_4}} \\ r_6 = \overline{\overline{r_5} \cdot \overline{r_4\pi_5} \cdot \overline{r_3\pi_4\pi_5} \cdot \overline{r_2\pi_3\pi_4\pi_5} \cdot \overline{r_1\pi_2\pi_3\pi_4\pi_5} \cdot \overline{e\pi_1\pi_2\pi_3\pi_4\pi_5}} \end{array} \right.$$

Изобразим на рисунке 6 схему блока переноса I яруса

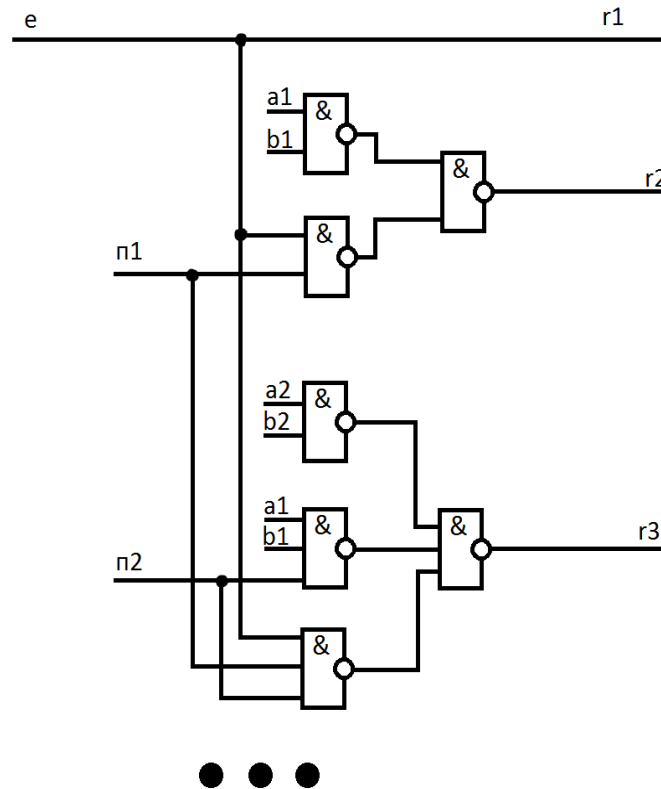


Рисунок 6. Схема блока переноса I яруса

Задержка построенного блока переноса I-го яруса равна  $T_I = 2 \cdot \tau$

Код моделирования I-го яруса переноса:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
```

```

entity Block_carry_I is
  port(e: in std_logic; PI, GEN: in std_logic_vector(5 downto 0); r: out std_logic_vector(5 downto 1));
end Block_carry_I;

architecture arch_Block_carry_I of Block_carry_I is
  component NAND1 is
    port(x1: in std_logic; y: out std_logic);
  end component NAND1;

  component NAND2 is
    port(x1, x2: in std_logic; y: out std_logic);
  end component NAND2;

  component NAND3 is
    port(x1, x2, x3: in std_logic; y: out std_logic);
  end component NAND3;

  component NAND4 is
    port(x1, x2, x3, x4: in std_logic; y: out std_logic);
  end component NAND4;

  component NAND5 is
    port(x1, x2, x3, x4, x5: in std_logic; y: out std_logic);
  end component NAND5;

  component NAND6 is
    port(x1, x2, x3, x4, x5, x6: in std_logic; y: out std_logic);
  end component NAND6;

  signal r2_1, r2_2: std_logic;
  signal r3_1, r3_2, r3_3: std_logic;
  signal r4_1, r4_2, r4_3, r4_4: std_logic;
  signal r5_1, r5_2, r5_3, r5_4, r5_5: std_logic;
  signal r6_1, r6_2, r6_3, r6_4, r6_5, r6_6: std_logic;

begin

  RR2_1: NAND1 port map (GEN(0), r2_1);
  RR2_2: NAND2 port map (e, PI(0), r2_2);
  RR2_3: NAND2 port map (r2_1, r2_2, r(1));--

  RR3_1: NAND1 port map (GEN(1), r3_1);
  RR3_2: NAND2 port map (GEN(0), PI(1), r3_2);
  RR3_3: NAND3 port map (e, PI(0), PI(1), r3_3);
  RR3_4: NAND3 port map (r3_1, r3_2, r3_3, r(2));--

  RR4_1: NAND1 port map (GEN(2), r4_1);
  RR4_2: NAND2 port map (GEN(1), PI(2), r4_2);
  RR4_3: NAND3 port map (GEN(0), PI(1), PI(2), r4_3);
  RR4_4: NAND4 port map (e, PI(0), PI(1), PI(2), r4_4);
  RR4_5: NAND4 port map (r4_1, r4_2, r4_3, r4_4, r(3));--

  RR5_1: NAND1 port map (GEN(3), r5_1);
  RR5_2: NAND2 port map (GEN(2), PI(3), r5_2);
  RR5_3: NAND3 port map (GEN(1), PI(2), PI(3), r5_3);
  RR5_4: NAND4 port map (GEN(0), PI(1), PI(2), PI(3), r5_4);
  RR5_5: NAND5 port map (e, PI(0), PI(1), PI(2), PI(3), r5_5);

```

RR5\_6: NAND5 port map (r5\_1, r5\_2, r5\_3, r5\_4, r5\_5, r(4));--

RR6\_1: NAND1 port map (GEN(4), r6\_1);

RR6\_2: NAND2 port map (GEN(3), PI(4), r6\_2);

RR6\_3: NAND3 port map (GEN(2), PI(3), PI(4), r6\_3);

RR6\_4: NAND4 port map (GEN(1), PI(2), PI(3), PI(4), r6\_4);

RR6\_5: NAND5 port map (GEN(0), PI(1), PI(2), PI(3), PI(4), r6\_5);

RR6\_6: NAND6 port map (e, PI(0), PI(1), PI(2), PI(3), PI(4), r6\_6);

RR6\_7: NAND6 port map (r6\_1, r6\_2, r6\_3, r6\_4, r6\_5, r6\_6, r(5));--

end arch\_Block\_carry\_I;

Построим блок суммы:

 


Рисунок 7. Схема блока суммы

Функция:

$$S_i = \overline{(a_i b_i \vee \bar{a}_i \bar{b}_i)} r_{i-1} \vee \overline{(a_i \bar{b}_i \vee \bar{a}_i b_i)} \bar{r}_{i-1}$$

Задержка сумматора равна  $T_{\text{одн.см}} = 2 \cdot \tau$

Код моделирования блока суммы:

library IEEE;

use IEEE.STD\_LOGIC\_1164.all;

entity Basic\_adder is

port(r, a, b: in std\_logic; s: out std\_logic);

end Basic\_adder;

architecture arch\_Basic\_adder of Basic\_adder is

component NAND1 is

```

    port(x1: in std_logic; y: out std_logic);
end component NAND1;

component AND2_OR2_NOT is
    port(x1, x2, x3, x4: in std_logic; y: out std_logic);
end component AND2_OR2_NOT;

signal tmp1, tmp2, not_r, not_a, not_b: std_logic;

begin
    -- 'NOT a' and 'NOT b' are without delays (we counted it yearlier)
    not_a <= not a;
    not_b <= not b;
    NOTR: NAND1 port map (r, not_r);
    COMP1: AND2_OR2_NOT port map (a, b, not_a, not_b, tmp1);
    COMP2: AND2_OR2_NOT port map (a, not_b, b, not_a, tmp2);
    COMP3: AND2_OR2_NOT port map (r, tmp1, tmp2, not_r, s);

end arch_Basic_adder;

```

## 6. Синтез многоразрядного сумматора и получение схемы для тестирования

Применим полученные блоки переносов и одноразрядные сумматоры для создания 12-ти разрядного сумматора.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity Adder_12digits is
    port(A,B: in std_logic_vector(11 downto 0);
         S_out: out std_logic_vector(11 downto 0));
end Adder_12digits;

architecture arch_Adder_12digits of Adder_12digits is

    component PI_and_GEN is
        port(A, B: in std_logic_vector(11 downto 0); PI_out, GEN_out: out std_logic_vector(11 downto 0));
    end component PI_and_GEN;

    component Block_Carry_II is
        port(g: in std_logic; PI, GEN: in std_logic_vector(5 downto 0); E: out std_logic);
    end component Block_carry_II;

    component Block_Carry_I is
        port(e: in std_logic; PI, GEN: in std_logic_vector(5 downto 0); r: out std_logic_vector(5 downto 1));
    end component Block_carry_I;

    component Basic_adder is
        port(R: in std_logic; A, B: in std_logic; S: out std_logic);

```

```

end component Basic_adder;

signal PI: std_logic_vector(11 downto 0);
signal GEN: std_logic_vector(11 downto 0);
signal E1: std_logic;
signal R: std_logic_vector(11 downto 0);

begin

    COMP_PI_AND_GEN: PI_and_GEN port map (A(11 downto 0), B(11 downto 0), PI(11 downto 0),
    GEN(11 downto 0));

    COMP_CARRY_II: Block_Carry_II port map ('0', PI(5 downto 0), GEN(5 downto 0), E1);

    R(0) <= '0';
    COMP1_CARRY_I: Block_Carry_I port map ('0', PI(5 downto 0), GEN(5 downto 0), R(5 downto 1));
    R(6) <= E1;
    COMP2_CARRY_I: Block_Carry_I port map (E1, PI(11 downto 6), GEN(11 downto 6), R(11 downto
    7));

    COMP0_ADDER: Basic_adder port map ('0', A(0), B(0), S_out(0));
    COMP1_ADDER: Basic_adder port map (R(1), A(1), B(1), S_out(1));
    COMP2_ADDER: Basic_adder port map (R(2), A(2), B(2), S_out(2));
    COMP3_ADDER: Basic_adder port map (R(3), A(3), B(3), S_out(3));
    COMP4_ADDER: Basic_adder port map (R(4), A(4), B(4), S_out(4));
    COMP5_ADDER: Basic_adder port map (R(5), A(5), B(5), S_out(5));
    COMP6_ADDER: Basic_adder port map (R(6), A(6), B(6), S_out(6));
    COMP7_ADDER: Basic_adder port map (R(7), A(7), B(7), S_out(7));
    COMP8_ADDER: Basic_adder port map (R(8), A(8), B(8), S_out(8));
    COMP9_ADDER: Basic_adder port map (R(9), A(9), B(9), S_out(9));
    COMP10_ADDER: Basic_adder port map (R(10), A(10), B(10), S_out(10));
    COMP11_ADDER: Basic_adder port map (R(11), A(11), B(11), S_out(11));

end arch_Adder_12digits;

```

Добавим к этой сущности реализацию регистров А и В, чтобы получить финальную версию устройства Adder.

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity Adder is
    port(clk: in std_logic;
          cin: in std_logic;
          a,b: in std_logic_vector(11 downto 0);
          s: out std_logic_vector(11 downto 0);
          cout: out std_logic);
end Adder;

architecture arch_Adder of Adder is

    component K155TM7_scheme_12digits is
        port(C: in std_logic; D: in std_logic_vector(11 downto 0); Q: out std_logic_vector(11 downto 0));

```



```

end component K155TM7_scheme_12digits;

component Adder_12digits is
  port(A,B: in std_logic_vector(11 downto 0);
        S_out: out std_logic_vector(11 downto 0));
end component Adder_12digits;

signal A_reg, B_reg: std_logic_vector(11 downto 0);

begin
  REGISTER_A: K155TM7_scheme_12digits port map (clk, a(11 downto 0), A_reg(11 downto 0));
  REGISTER_B: K155TM7_scheme_12digits port map (clk, b(11 downto 0), B_reg(11 downto 0));
  ADDER_AB: Adder_12digits port map (A_reg(11 downto 0), B_reg(11 downto 0), S(11 downto 0));

end arch_Adder;

```

## 7. Тестирование суммирующего устройства

Проведем несколько заранее заготовленных тестов для оценки правильности работы полученного сумматора.

Время подачи сигнала CLK в 40 нс обусловлено задержкой загрузки информации в регистры. 148 нс – максимальное время работы сумматора по условию.

Тест 1 – тест сумматора без переносов.

Тест 2 – тест сумматора без переносов при одном из нулевых чисел.

Тест 3 – проверка правильности переноса через все разряды.

Тест 4 – проверка правильности переноса до середины числа.

Тест 5, 6 – проверка работы сумматора на случайно заданных числах.

Код программы тестирования:

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

use std.textio.all;
use IEEE.numeric_std.all;

library osvvm;
use osvvm.RandomPkg.all;

entity Test_Adder is
end Test_Adder;

architecture arch_Test_Adder of Test_Adder is

```

```

component Adder is
  port(clk: in std_logic;
        cin: in std_logic;
        a,b: in std_logic_vector(11 downto 0);
        s: out std_logic_vector(11 downto 0);
        cout: out std_logic);
end component Adder;

signal clk, cin: std_logic;
signal a, b, s: std_logic_vector(11 downto 0);
signal cout: std_logic;

begin
  DUT: Adder port map (clk, cin, a, b, s, cout);
  process
    begin
-- Test 1
      clk <= '1';
      A <= "011011001001";
      B <= "100100110110";
      wait for 40 ns;
      clk <= '0';
      wait for 148 ns;

-- Test 2
      clk <= '1';
      A <= "000000000000";
      B <= "111111111111";
      wait for 40 ns;
      clk <= '0';
      wait for 148 ns;

-- Test 3
      clk <= '1';
      A <= "011111111111";
      B <= "000000000001";
      wait for 40 ns;
      clk <= '0';
      wait for 148 ns;

-- Test 4
      clk <= '1';
      A <= "011111011111";
      B <= "000000000001";
      wait for 40 ns;
      clk <= '0';
      wait for 148 ns;

-- Test 5 - random digits
      clk <= '1';
      A <= "011010101111";
      B <= "000111100110";
      --expected: 100010010101
      wait for 40 ns;
      clk <= '0';
      wait for 148 ns;
    end process;
  end

```

```

-- Test 6 - random digits
  clk <= '1';
  A <= "000110101010";
  B <= "001011000111";
  --expected: 10001110001
  wait for 40 ns;
  clk <= '0';
  wait for 148 ns;

end process;
end arch_Test_Adder;

```

Диаграмма тестов №1-3 представлена на рисунке 8.

 


Рисунок 8. Тесты №1-3

Диаграмма тестов №4-6 представлена на рисунке 9.

 


Рисунок 9. Тесты №4-6

Тестирование устройства с помощью случайных чисел и автоматической проверки.

Код программы:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use std.textio.all;
use IEEE.numeric_std.all;

library osvvm;
use osvvm.RandomPkg.all;

entity Test_Adder is

```

```
end Test_Adder;
```

architecture arch\_Test\_Adder of Test\_Adder is

```
component Adder is
```

```
port(clk: in std_logic;
```

```
cin: in std_logic;
```

```
a,b: in std_logic_vector(11 downto 0);
```

```
s: out std_logic_vector(11 downto 0);
```

```
cout: out std_logic);
```

```
end component Adder;
```

```
signal testa, testb, testResult, result: std_logic_vector(11 downto 0);
```

```
signal c: std_logic;
```

```
signal cin_empty, cout_empty: std_logic;
```

```
begin
```

```
dut: adder port map(c, cin_empty, testA, testB, result, cout_empty);
```

```
gen_rand: process
```

```
variable rA, rB: RandomPType;
```

```
variable randA, randB, b: integer;
```

```
variable L: line;
```

```
begin
```

```
randA := rA.RandInt(0, 4095);
```

```
randB := rB.RandInt(0, 4095);
```

```
testA <= std_logic_vector(to_unsigned(randA, 12));
```

```
testB <= std_logic_vector(to_unsigned(randB, 12));
```

```
testResult <= std_logic_vector(to_unsigned(randA+randB, testResult'length));
```

```
c <= '1';
```

```
wait for 40 ns;
```

```
c <= '0';
```

```
wait for 148 ns;
```

```
if (testResult = result) then
```

```
write(L, string("Success"));
```

```
else
```

```
write(L, string("Error"));
```

```
end if;
```

```
end process;
```

```
end arch_Test_Adder;
```

Результат моделирования на рисунке :


 


Рисунок 10. Тестирование с автоматической проверкой

 8. Нахождение критического пути сумматора



## Рисунок 11. Нахождение критического пути

Для поиска используем тест переноса через все разряды числа.  
Задержка критического пути составила 140 нс (40 нс – задержка регистров) < 148 нс. Условие задания выполнено.

## 9. Вывод

В ходе выполнения работы было смоделировано многоразрядное суммирующее устройство, которое прошло необходимые тесты и прошло по условию максимальной задержки.